

4 BIT MULTIPLIER

INTRODUCTION

A 4-bit multiplier is a digital circuit that multiplies two 4-bit binary numbers, producing an 8-bit output. It uses logic gates such as AND gates and adders to perform binary multiplication efficiently. Commonly used in microprocessors, arithmetic units, and embedded systems, the 4-bit multiplier is valued for its simplicity, speed, and low power consumption, making it a crucial building block in more complex digital systems.

OBJECTIVE

The objective of a 4-bit multiplier is to:

1. Multiply two 4-bit binary numbers.
2. Produce an 8-bit binary output.
3. Ensure accuracy using logic gates.
4. Optimize for speed and efficiency in digital circuits.
5. Serve as a building block for larger multipliers.

SCOPE


The scope of a 4-bit multiplier involves:

1. **Basic Arithmetic:** Used in microprocessors and ALUs for binary multiplication.
2. **Embedded Systems:** Applied in low-power, simple devices.
3. **Signal Processing:** Used in DSPs for filtering and encoding.
4. **Educational Tool:** Foundation for understanding larger multipliers.
5. **Scalability:** Expandable for higher-bit multipliers.
6. **Hardware Optimization:** Applied in efficient FPGA and ASIC designs.

It plays a vital role in digital circuits and low-complexity applications.

BLOCK DIAGRAM

4 BIT BY 4 BIT BINARY MULTIPLIER

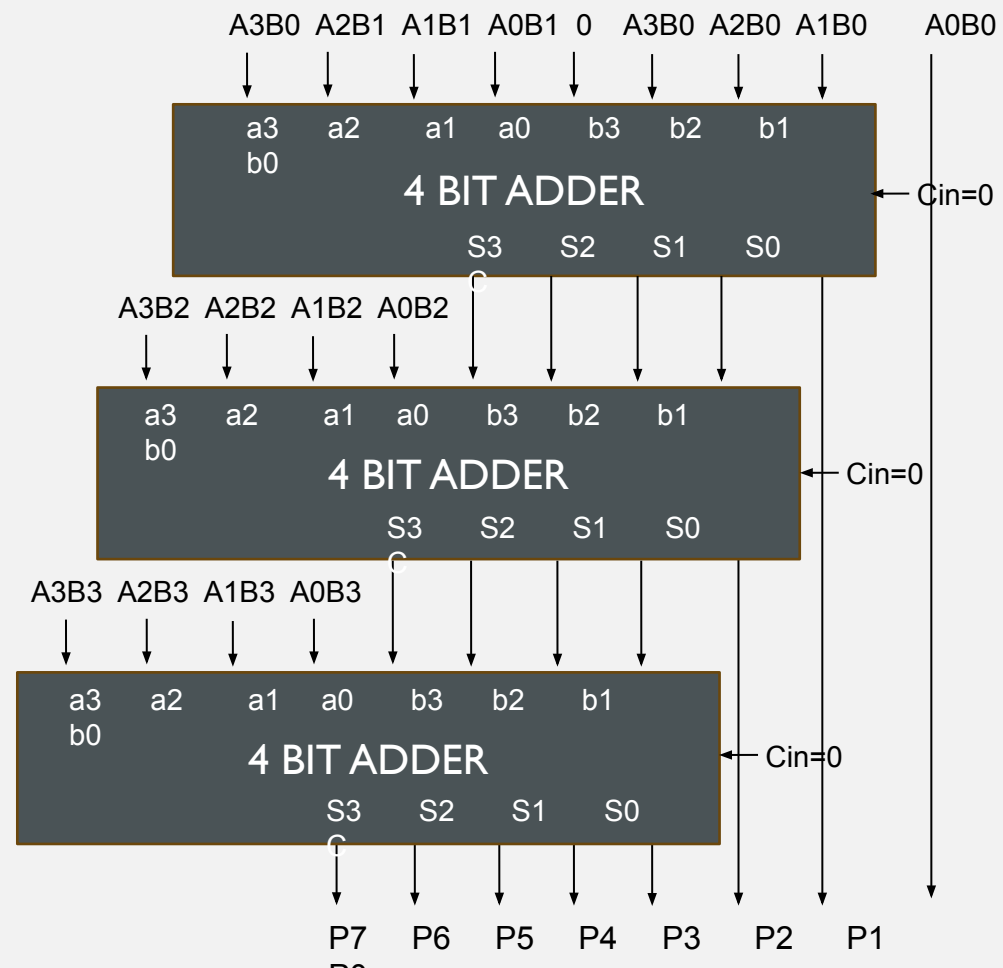

DESIGN

A 4-bit multiplier multiplies two 4-bit binary numbers using logic gates and adders.

1. **Inputs:** Two 4-bit numbers: A ($A_3 A_2 A_1 A_0$) and B ($B_3 B_2 B_1 B_0$).
2. **Partial Products:** Generated by multiplying each bit of A with each bit of B using AND gates.
3. **Summation:** The partial products are summed using half adders and full adders.
4. **Output:** The final result is an 8-bit binary output: $P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0$.

This design efficiently performs binary multiplication and is commonly used in digital systems like microprocessors.

```
1 module multiplier_4bit(  
2     input [3:0] a, // 4-bit input a  
3     input [3:0] b, // 4-bit input b  
4     output [7:0] product // 8-bit output product  
5 );  
6     assign product = a * b; // Multiplication operation  
7 endmodule
```

```
1 module testbench;
2   reg [3:0] a, b;
3   wire [7:0] product;
4
5   // Instantiate the multiplier module
6   multiplier_4bit uut (
7     .a(a),
8     .b(b),
9     .product(product)
10  );
11
12  // Dump the variables into a .vcd file for GTKWave
13  initial begin
14    $dumpfile("multiplier_4bit.vcd"); // Create a VCD file
15    $dumpvars(0, testbench); // Dump all signals in the testbench
16  end
17
18  initial begin
19    // Test cases
20    $monitor("a = %b, b = %b, product = %b", a, b, product);
21
```



```
22 // First test
23 a = 4'b0011; b = 4'b0101; // 3 * 5
24 #10;
25
26 // Second test
27 a = 4'b1111; b = 4'b1111; // 15 * 15
28 #10;
29
30 // Third test
31 a = 4'b1001; b = 4'b0110; // 9 * 6
32 #10;
33
34 $finish;
35 end
36 endmodule
```

SOFTWARE REQUIREMENTS

1. **HDL Design Tools:** icarus Verilog or VHDL
2. **Simulation Tools:** Xilinx Vivado, ModelSim, or Quartus Prime
3. **Schematic Design Software:** Multisim or Proteus
4. **FPGA/ASIC Design Tools:** Xilinx ISE or Altera Quartus
5. **Circuit Design and Verification:** LTspice or Cadence


HARDWARE REQUIREMENTS

1. **4-Bit Adder IC (Binary Adder):** IC 7483
2. **Logic Gates (if not using 4-bit adder IC):** AND Gates (7408), OR Gates (7432), XOR Gates (7486), NOT Gates (7404)
3. **Flip-Flops or Registers (Optional):** IC 7474 (D Flip-Flop)
4. **Power Supply:** Typically, 5V DC is required to power the ICs
5. **Breadboard or PCB (Printed Circuit Board)**
6. **Jumper Wires**
7. **Input Devices:** Toggle Switches or DIP Switches
8. **Output Devices:** LEDs, 7-Segment Display (optional)
9. **Oscilloscope or Logic Analyzer**
10. **Resistors:** **330 Ω or 220 Ω resistors** to limit current through the LEDs (if used for output display).
11. **FPGA Development Board** (if implementing in HDL): If you're designing the 4-bit adder digitally, a board like Xilinx or Altera FPGA will be required to synthesize and test the design in hardware.

BOM

1. **ICs:**
 - 1 x IC 7483
 - 1 x IC 7408
 - 1 x IC 7486
 - 1 x IC 7432
2. **Discrete Components:**
 - Resistors: 4 x 330 Ω (LEDs), 4 x 1k Ω (pull-ups)
 - Capacitors: 2 x 0.1 μ F (decoupling)
3. **Input/Output:**
 - 4 x LEDs: Output display
 - 4 x Switches: Binary input
 - 1 x 7-Segment Displays (optional)
4. **Power Supply:**
 - 5V DC power source
5. **Prototyping Accessories:**
 - 1 x Breadboard
 - Jumper Wires
6. **Testing Equipment:**
 - 1 x Oscilloscope/Logic Analyzer

SIMULATION OUTPUT

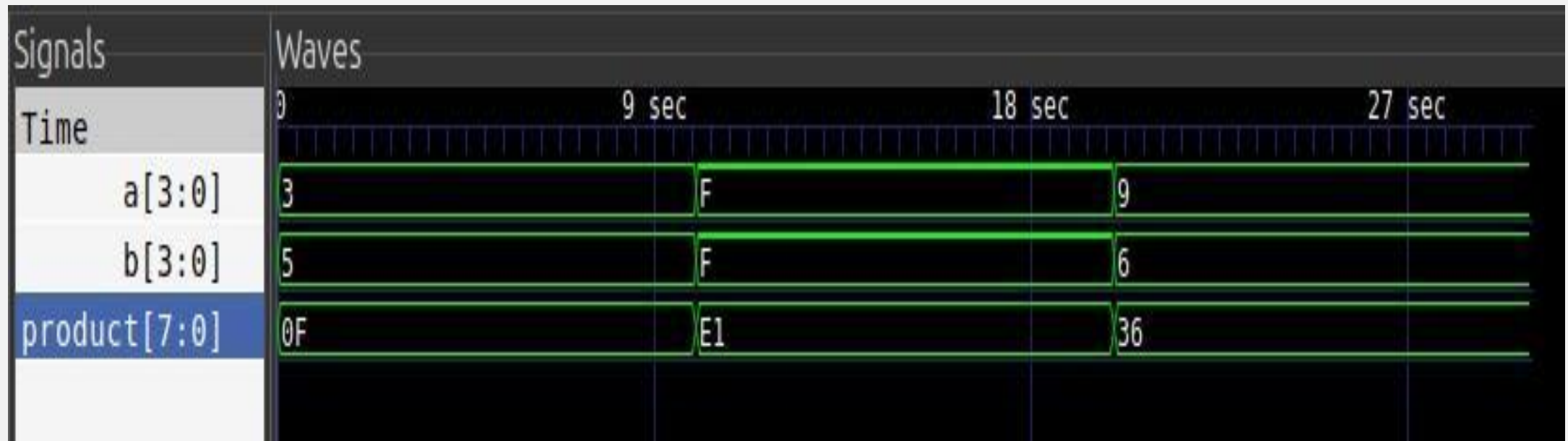

```
gedit multiplier_4bit.v
gedit testbench.v
iverilog -o multiplie_4bit1 testbench.v multiplier_4bit.v

vvp multiplie_4bit1
VCD info: dumpfile multiplier_4bit.vcd opened for output.
a = 0011, b = 0101, product = 00001111
a = 1111, b = 1111, product = 11100001
a = 1001, b = 0110, product = 00110110
testbench.v:34: $finish called at 30 (1s)
```


```
gtkwave multiplier_4bit.vcd
```

```
GTKWave Analyzer v3.3.116 (w) 1999-2023 BSI
```


```
[0] start time.
```

```
[30] end time.
```

FPGA IMPLEMENTATION

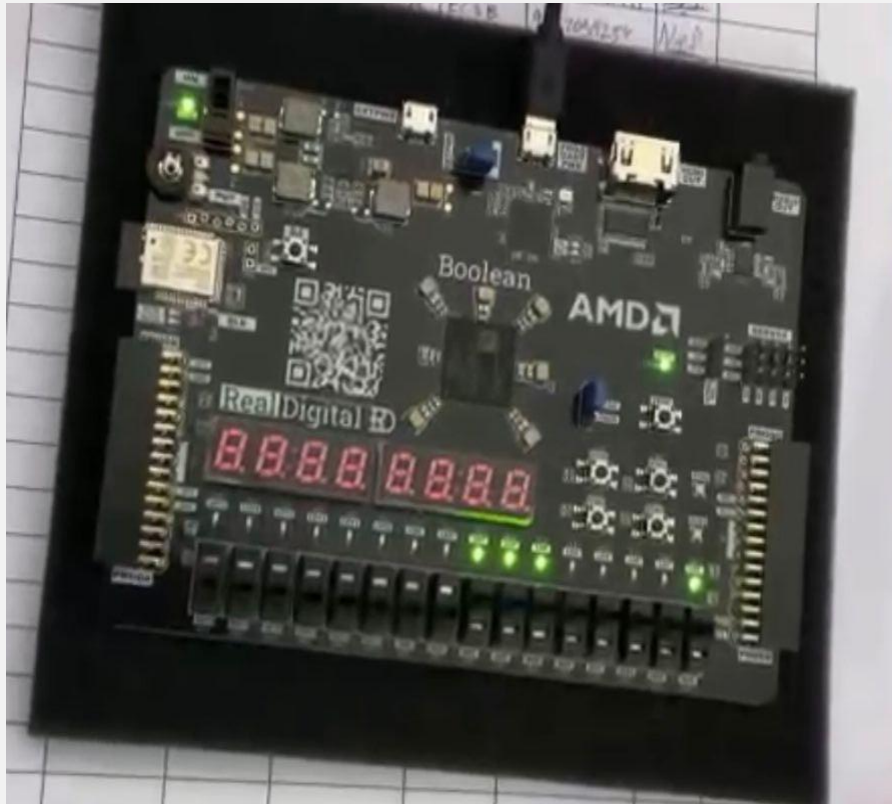

$$15 * 15 = 225$$

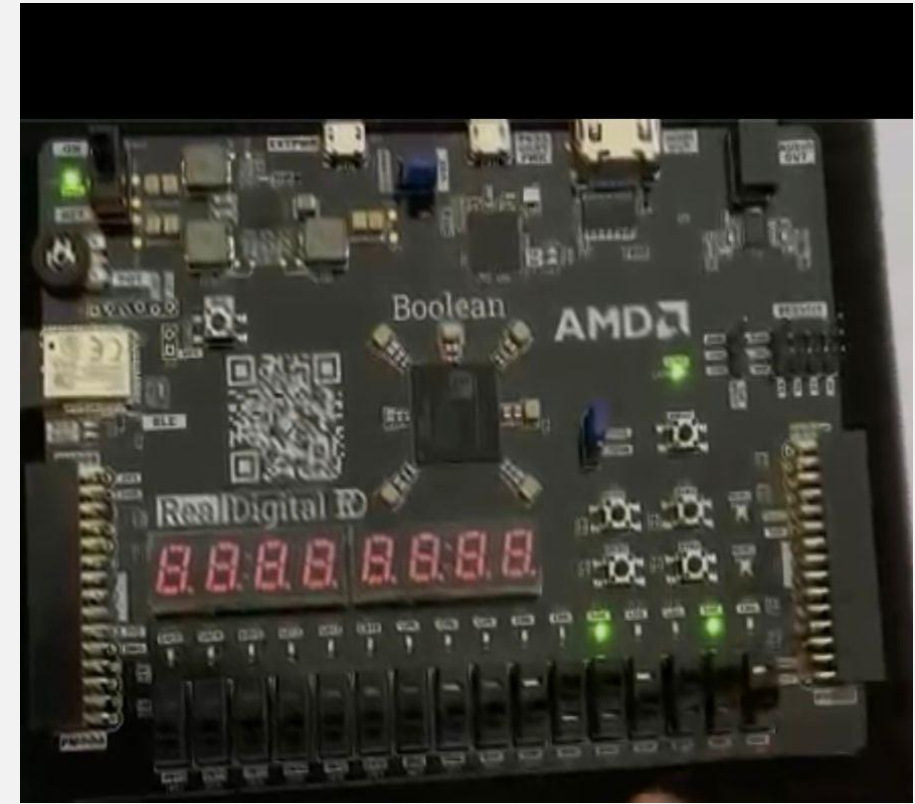

$$3 * 6 = 18$$

CONCLUSION

- The 4-bit multiplier is crucial in digital computation, providing efficient and reliable multiplication of binary numbers. Its ability to produce accurate 8-bit results from two 4-bit inputs makes it ideal for integration into systems such as microprocessors and arithmetic units.
- Moreover, its scalability allows for expansion into larger multipliers, making it a versatile solution for more complex circuit designs.
- Overall, the 4-bit multiplier enhances digital systems by offering a balance of precision and efficiency in performing arithmetic operations.

REFERENCES

- [1] A. Kumar and B. Patel, "Design and Implementation of a 4-Bit Multiplier System," International Journal of Electronics and Communication Engineering.
- [2] M. Johnson, "Utilizing Multipliers in Digital Systems," Proceedings of the IEEE International Conference on Digital Systems

THANK YOU